

LAB-3 4 Bit Adder

Deliverables:

- Implement a one bit full adder with carry in and carry out pin using Quartus II Schematic Block.
- Connect 4 one-bit full adder in series to get a 4-bit full adder.
- Compilation and Simulation on Quartus II
- Combine the 4 bit full adder with the 7 segment display and test it on DE2 Board.

Binary Addition

- Binary 1 bit addition
 - $0 + 0 = 0$
 - $1 + 0 = 1$
 - $0 + 1 = 1$
 - $1 + 1 = 0$ with carry out of 1.
- When implement adder using logic gates, we need to add the carry input (from the previous bit) and carry out output. Eg.

| Carry In | Carry Out | Carry In | Carry Out | Carry In |
|----------|-----------|----------|-----------|----------|
| 1 | 0 | 0 | | |
| 1 | 1 | 0 | 1 | |
| + 1 | 1 | 1 | 0 | |
| <hr/> | | | | |
| 1 | 1 | 0 | 1 | 1 |

Carry Out

1 Bit Full Adder

| X | Y | Cin | Sum | Cout |
|---|---|-----|-----|------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |



| XY \ Cin | | 00 | 01 | 11 | 10 |
|----------|---|----|----|----|----|
| Cin | 0 | | | | |
| | 1 | | | | |


Sum = ????

| XY \ Cin | | 00 | 01 | 11 | 10 |
|----------|---|----|----|----|----|
| Cin | 0 | | | | |
| | 1 | | | | |


Cout = ????

4 Bit Adder

- Block diagram of a 4 bit adder .

 


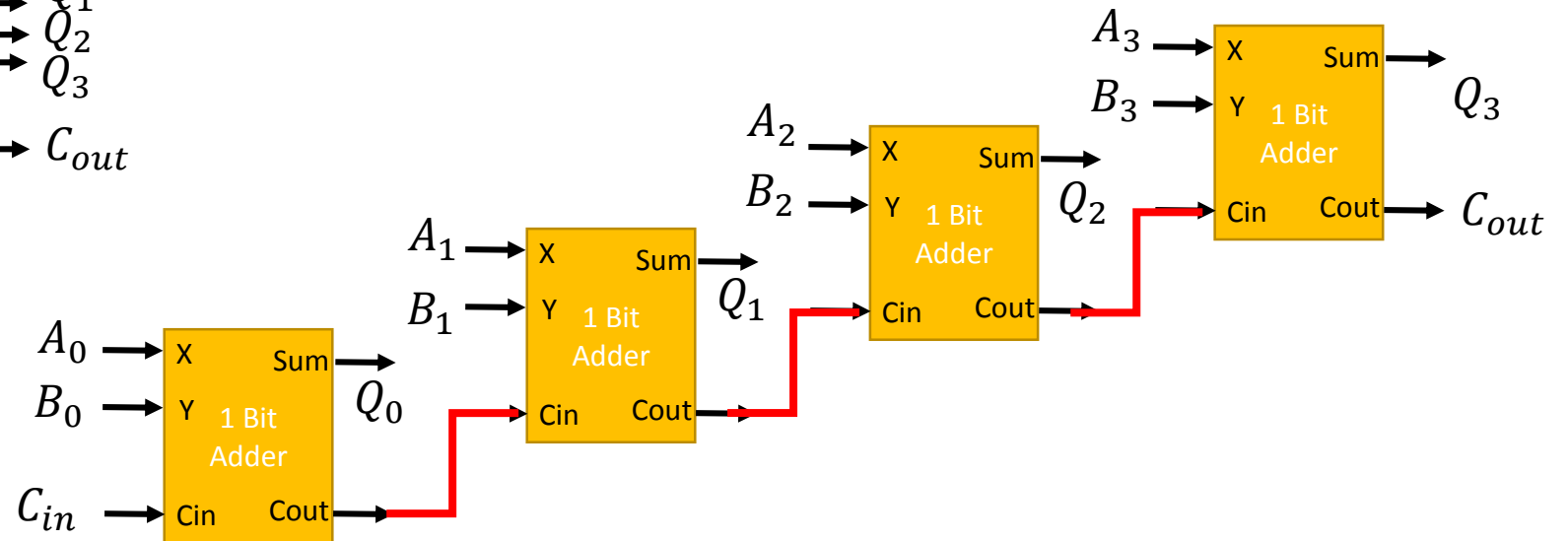- Four 1 bit adder in series to get a 4 bit adder.




Creating a symbol block

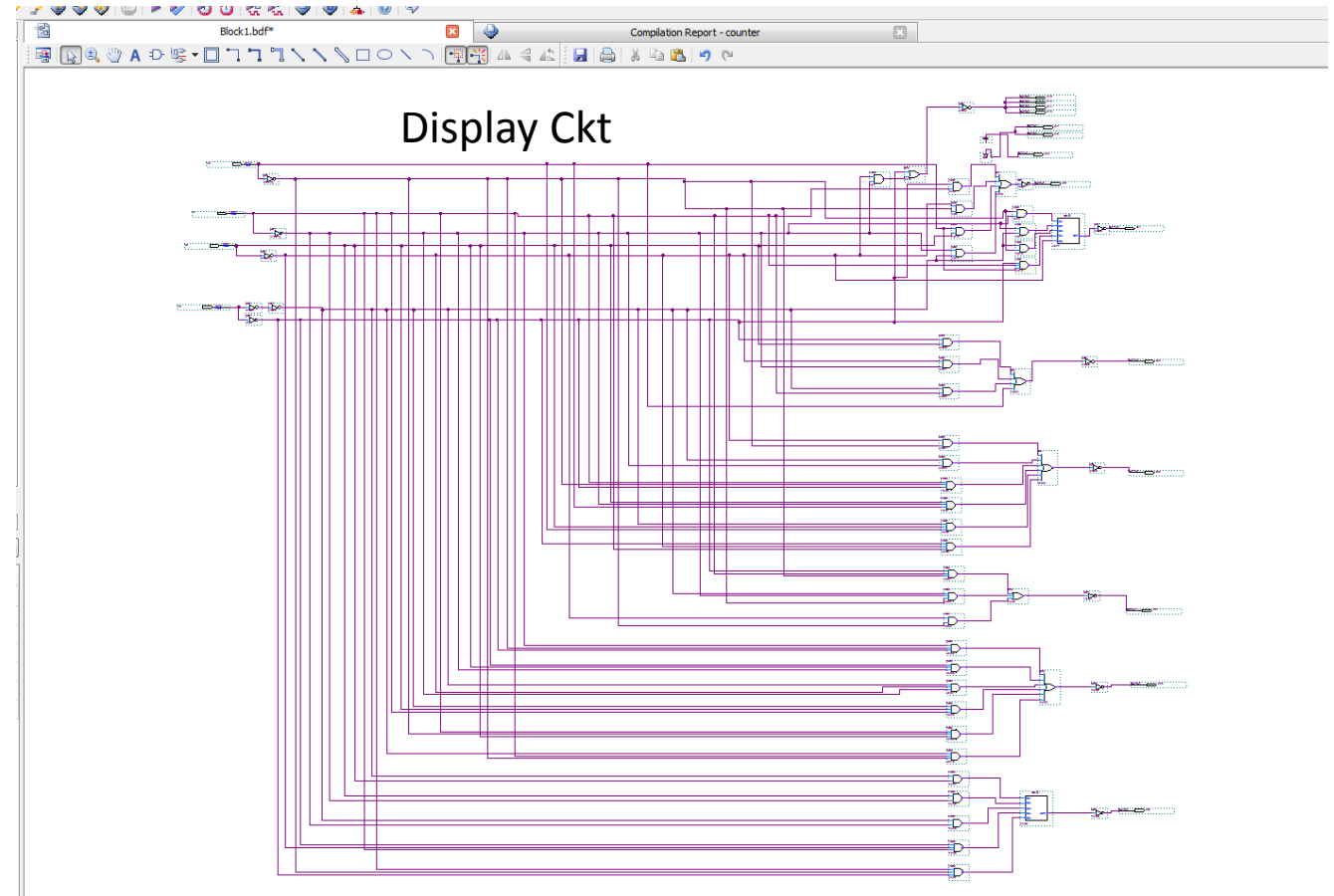- We can reuse the previous ckt in a new project instead of inserting the whole ckt.
- we can create the existing ckt to a symbol block and adding in other project as a block.



Creating a symbol block

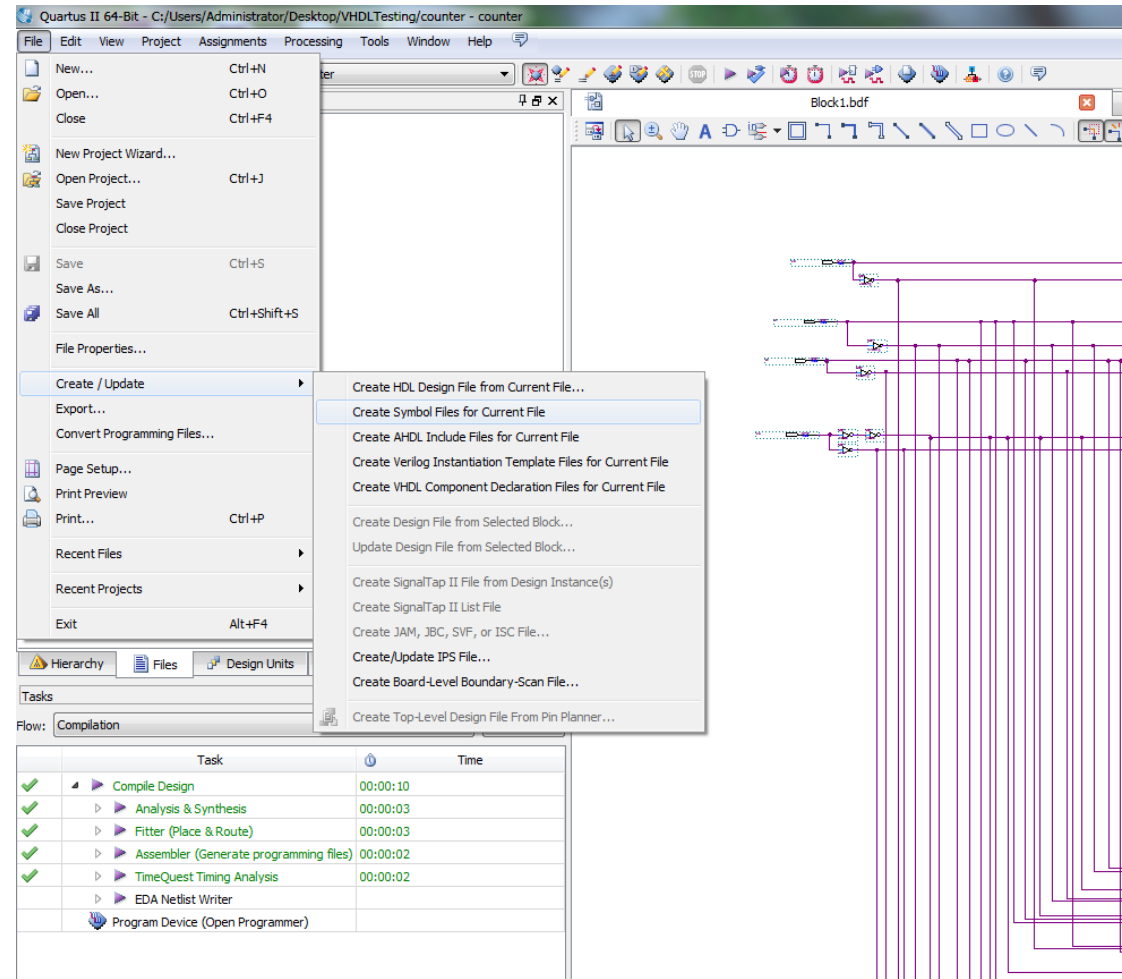
- File -> Create/Update -> Create Symbol Files for current file
- save the symbol file in your project folder. This will create a .bsf file.




Adding Existing Ckt as a symbol to new project.

- Create a new Schematic Block file and Open Symbol window from **Right Click-> Insert -> Symbol**.


1.

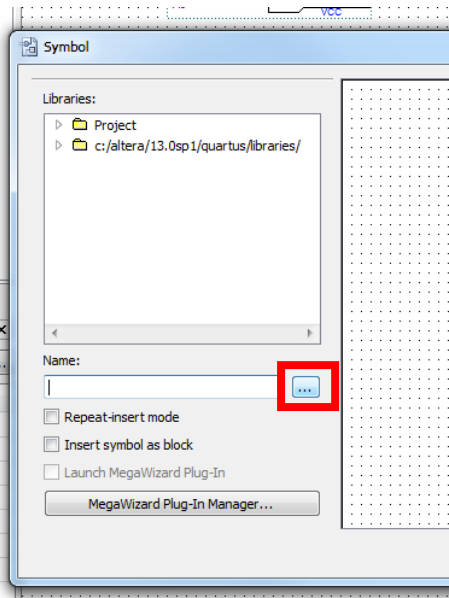


2. Select the desired .bsf file.

 

3. Eg. Display Ckt as a symbol block


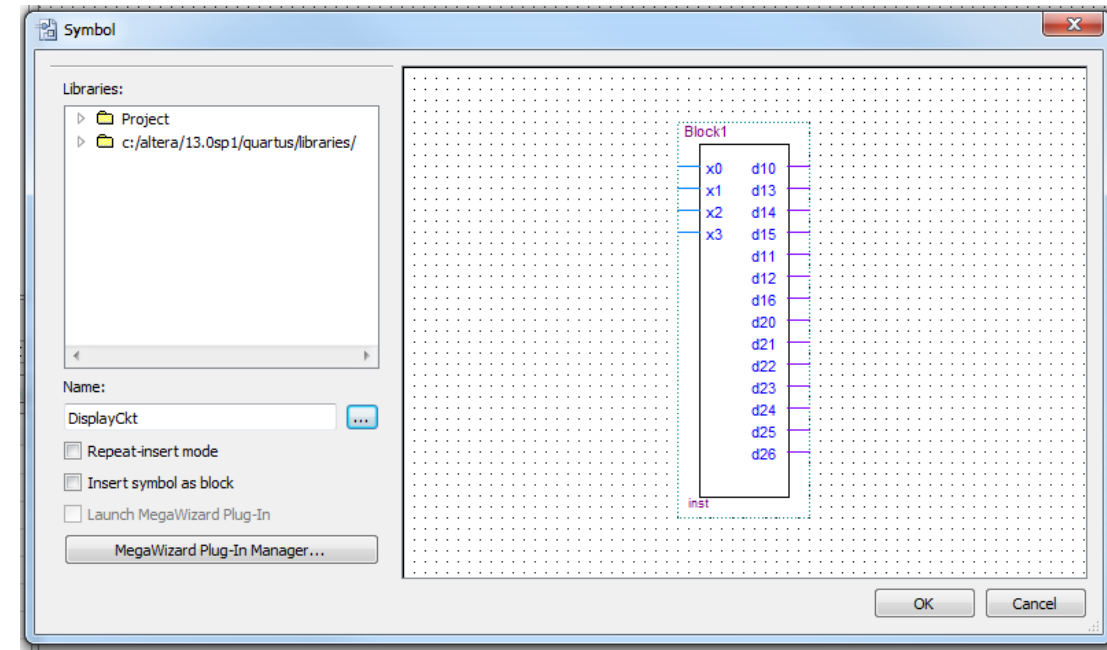


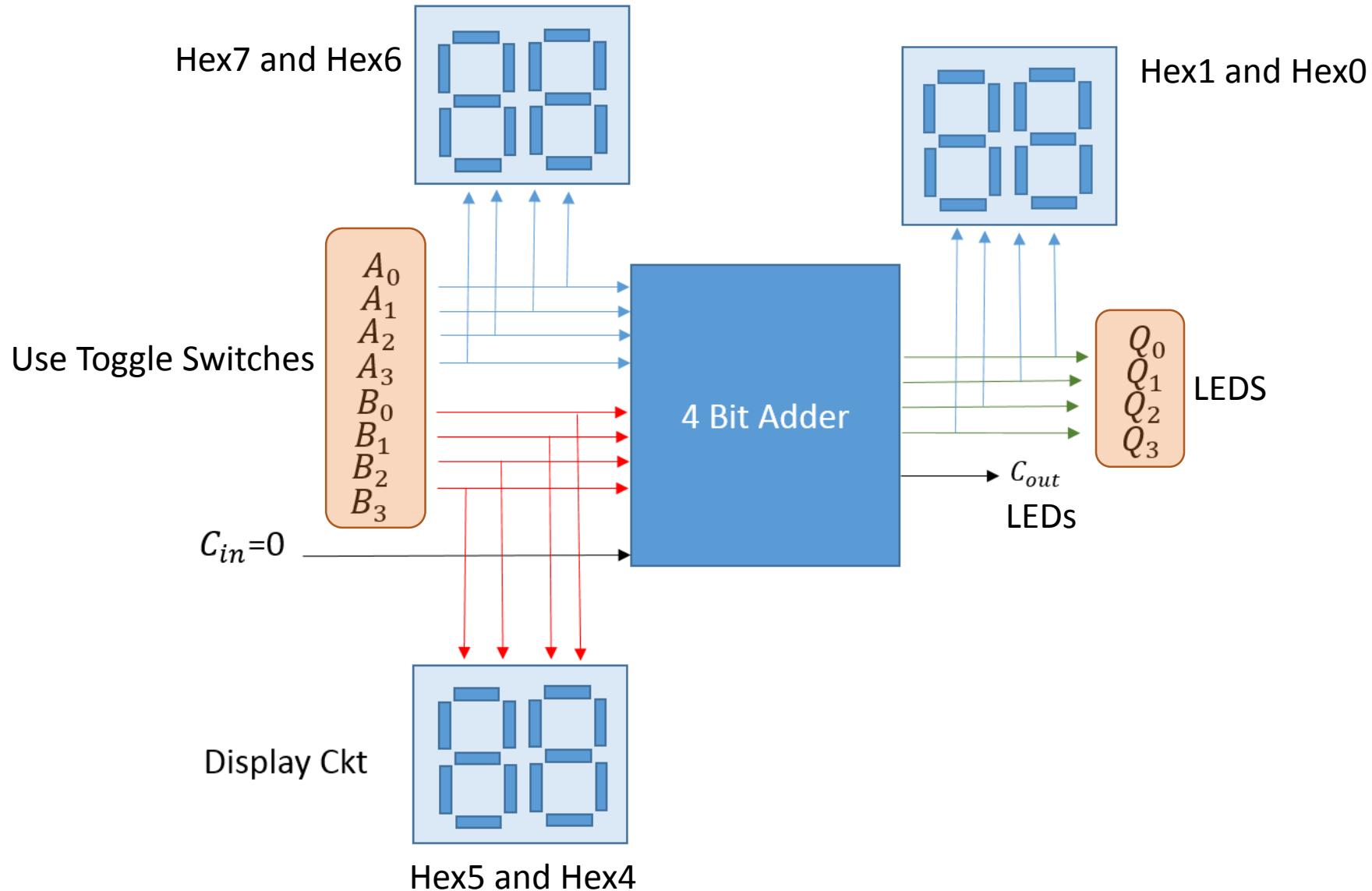Toplevel Ckt - 4 Bit Adder and Display Ckt




Compilation and Simulation

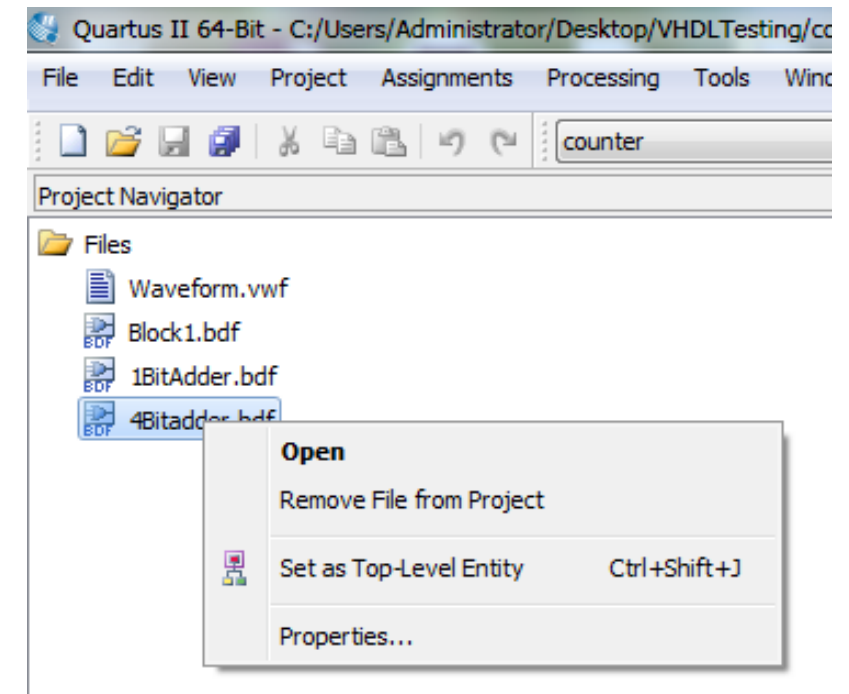 - When you have multiple .bdf files and to simulate a specific file.
- Right Click on the file you want to simulate and
- Select “**Set as Top-Level Entity**” and Compile.



Lab Implementation Flow Chart

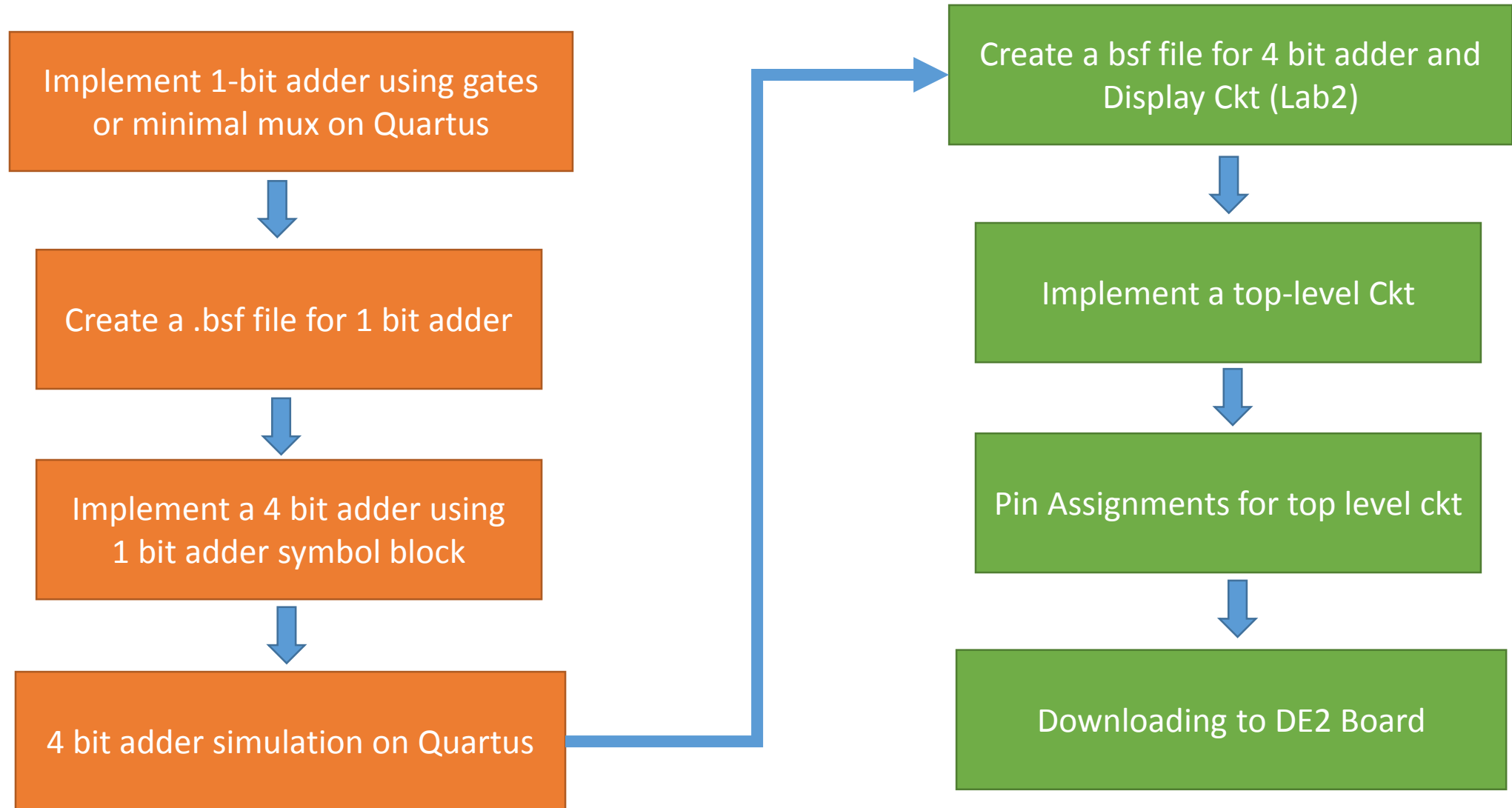

DE 2 Pin Table

| Signal Name | FPGA Pin No. |
|-------------|--------------|
| SW[0] | PIN_N25 |
| SW[1] | PIN_N26 |
| SW[2] | PIN_P25 |
| SW[3] | PIN_AE14 |
| SW[4] | PIN_AF14 |
| SW[5] | PIN_AD13 |
| SW[6] | PIN_AC13 |
| SW[7] | PIN_C13 |
| SW[8] | PIN_B13 |
| SW[9] | PIN_A13 |
| SW[10] | PIN_N1 |
| SW[11] | PIN_P1 |
| SW[12] | PIN_P2 |
| SW[13] | PIN_T7 |
| SW[14] | PIN_U3 |
| SW[15] | PIN_U4 |
| SW[16] | PIN_V1 |
| SW[17] | PIN_V2 |

| Signal Name | FPGA Pin No. |
|-------------|--------------|
| LEDR[0] | PIN_AE23 |
| LEDR[1] | PIN_AF23 |
| LEDR[2] | PIN_AB21 |
| LEDR[3] | PIN_AC22 |
| LEDR[4] | PIN_AD22 |
| LEDR[5] | PIN_AD23 |
| LEDR[6] | PIN_AD21 |
| LEDR[7] | PIN_AC21 |
| LEDR[8] | PIN_AA14 |
| LEDR[9] | PIN_Y13 |
| LEDR[10] | PIN_AA13 |
| LEDR[11] | PIN_AC14 |
| LEDR[12] | PIN_AD15 |
| LEDR[13] | PIN_AE15 |
| LEDR[14] | PIN_AF13 |
| LEDR[15] | PIN_AE13 |
| LEDR[16] | PIN_AE12 |
| LEDR[17] | PIN_AD12 |
| LEDG[0] | PIN_AE22 |
| LEDG[1] | PIN_AF22 |
| LEDG[2] | PIN_W19 |
| LEDG[3] | PIN_V18 |
| LEDG[4] | PIN_U18 |
| LEDG[5] | PIN_U17 |
| LEDG[6] | PIN_AA20 |
| LEDG[7] | PIN_Y18 |
| LEDG[8] | PIN_Y12 |

7 Segment Pin Table

| | |
|---------|----------|
| HEX0[0] | PIN_AF10 |
| HEX0[1] | PIN_AB12 |
| HEX0[2] | PIN_AC12 |
| HEX0[3] | PIN_AD11 |
| HEX0[4] | PIN_AE11 |
| HEX0[5] | PIN_V14 |
| HEX0[6] | PIN_V13 |
| HEX1[0] | PIN_V20 |
| HEX1[1] | PIN_V21 |
| HEX1[2] | PIN_W21 |
| HEX1[3] | PIN_Y22 |
| HEX1[4] | PIN_AA24 |
| HEX1[5] | PIN_AA23 |
| HEX1[6] | PIN_AB24 |
| HEX2[0] | PIN_AB23 |
| HEX2[1] | PIN_V22 |
| HEX2[2] | PIN_AC25 |
| HEX2[3] | PIN_AC26 |
| HEX2[4] | PIN_AB26 |
| HEX2[5] | PIN_AB25 |
| HEX2[6] | PIN_Y24 |
| HEX3[0] | PIN_Y23 |
| HEX3[1] | PIN_AA25 |
| HEX3[2] | PIN_AA26 |
| HEX3[3] | PIN_Y26 |
| HEX3[4] | PIN_Y25 |
| HEX3[5] | PIN_U22 |
| HEX3[6] | PIN_W24 |

| | |
|---------|--------|
| HEX4[0] | PIN_U9 |
| HEX4[1] | PIN_U1 |
| HEX4[2] | PIN_U2 |
| HEX4[3] | PIN_T4 |
| HEX4[4] | PIN_R7 |
| HEX4[5] | PIN_R6 |
| HEX4[6] | PIN_T3 |
| HEX5[0] | PIN_T2 |
| HEX5[1] | PIN_P6 |
| HEX5[2] | PIN_P7 |
| HEX5[3] | PIN_T9 |
| HEX5[4] | PIN_R5 |
| HEX5[5] | PIN_R4 |
| HEX5[6] | PIN_R3 |
| HEX6[0] | PIN_R2 |
| HEX6[1] | PIN_P4 |
| HEX6[2] | PIN_P3 |
| HEX6[3] | PIN_M2 |
| HEX6[4] | PIN_M3 |
| HEX6[5] | PIN_M5 |
| HEX6[6] | PIN_M4 |
| HEX7[0] | PIN_L3 |
| HEX7[1] | PIN_L2 |
| HEX7[2] | PIN_L9 |
| HEX7[3] | PIN_L6 |
| HEX7[4] | PIN_L7 |
| HEX7[5] | PIN_P9 |
| HEX7[6] | PIN_N9 |

Grading

| | Implementation | Report | Final Grade | Remark |
|--------------------------|----------------|--------|-------------|--------|
| Lab 1 | 7.5% | 7.5% | 15% | |
| Lab 2- Display Ckt | 7.5% | 7.5% | 15% | |
| Lab 3- 4 Bit Adder | 7.5% | 7.5% | 15% | |
| Lab 4 -4 Bit Subtractor | 7.5% | 7.5% | 15% | |
| Lab 5 – 4 Bit Multiplier | 7.5% | 7.5% | 15% | |
| Final Presentation | 7.5% | 7.5% | 10% | |
| Test 1 | | | 15% | |
| Total | | | 100% | |