

Lab 1B - Tone Generator

Implementation

LAB 1

Deliverables:

2. Tone generator:


- 555 timer to achieve an output signal with a base frequency $f_b = 16kHz$ and a duty cycle of 60%. Implement this circuit using the closest resistance values and capacitance available.

- Implement a circuit that will take this base frequency and divide it to

achieve a value $F_{out} = \begin{cases} \frac{1}{2(N+1)} f_b \\ \frac{1}{2(16-N)} f_b \end{cases}.$

- This circuit will accept a four-bit number N from the sequence generator implemented in part A. Use a 74LS169, and a 74LS76 J-K flip-flop to implement the T flip-flop.
- Connect the output of the previous circuit to a speaker through a capacitor.



Tone Generator

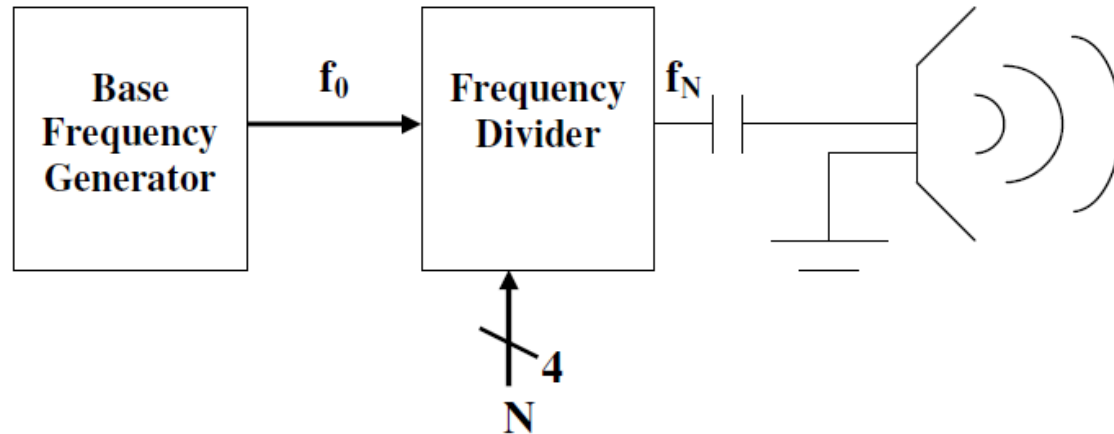

Frequency Generator:

555 Timer: The frequency and duty cycle are adjustable by varying the values of two biasing resistors and a capacitor. This IC is very flexible, being able to generate signals with a frequency range from well under 1Hz to 500kHz. We will use the 555 timer in its astable mode; that is, generating a signal that has a constant frequency.

Tone Generator(Contd.)

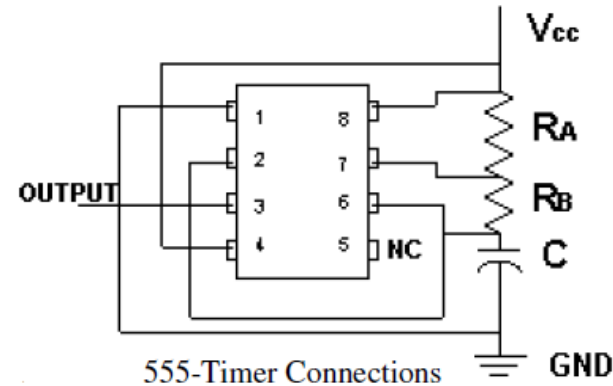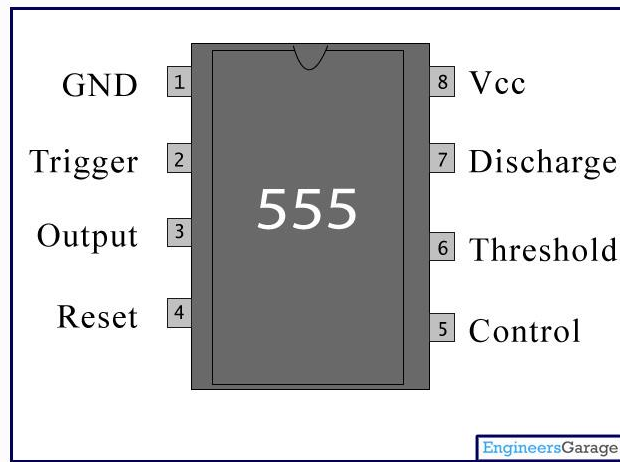

In astable mode, the 555 timer is connected as shown in Figure. Connected in this way, the output signal will have a high time:

$$t_H = 0.693 (R_A + R_B)C$$

And a low time:

$$t_L = 0.693 R_B C$$


The period of this signal is:

$$T = t_H + t_L \quad T = \frac{1}{\text{frequency}}$$

$$\text{duty cycle} = t_H / T * 100$$

Use $C = 10nF$.


74LS169 Modulo-N Counter

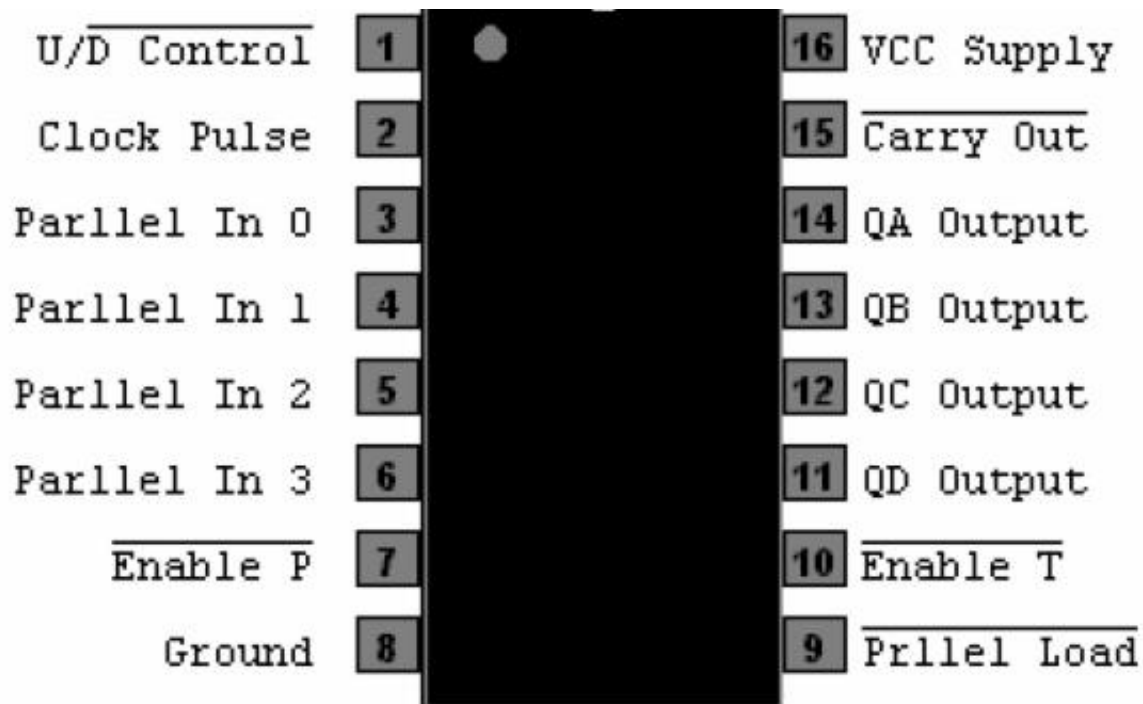


Output => Carry Out

Input => In0, In1, In2, In3 (Sequence generator outputs)

Enable P, Enable T => GND

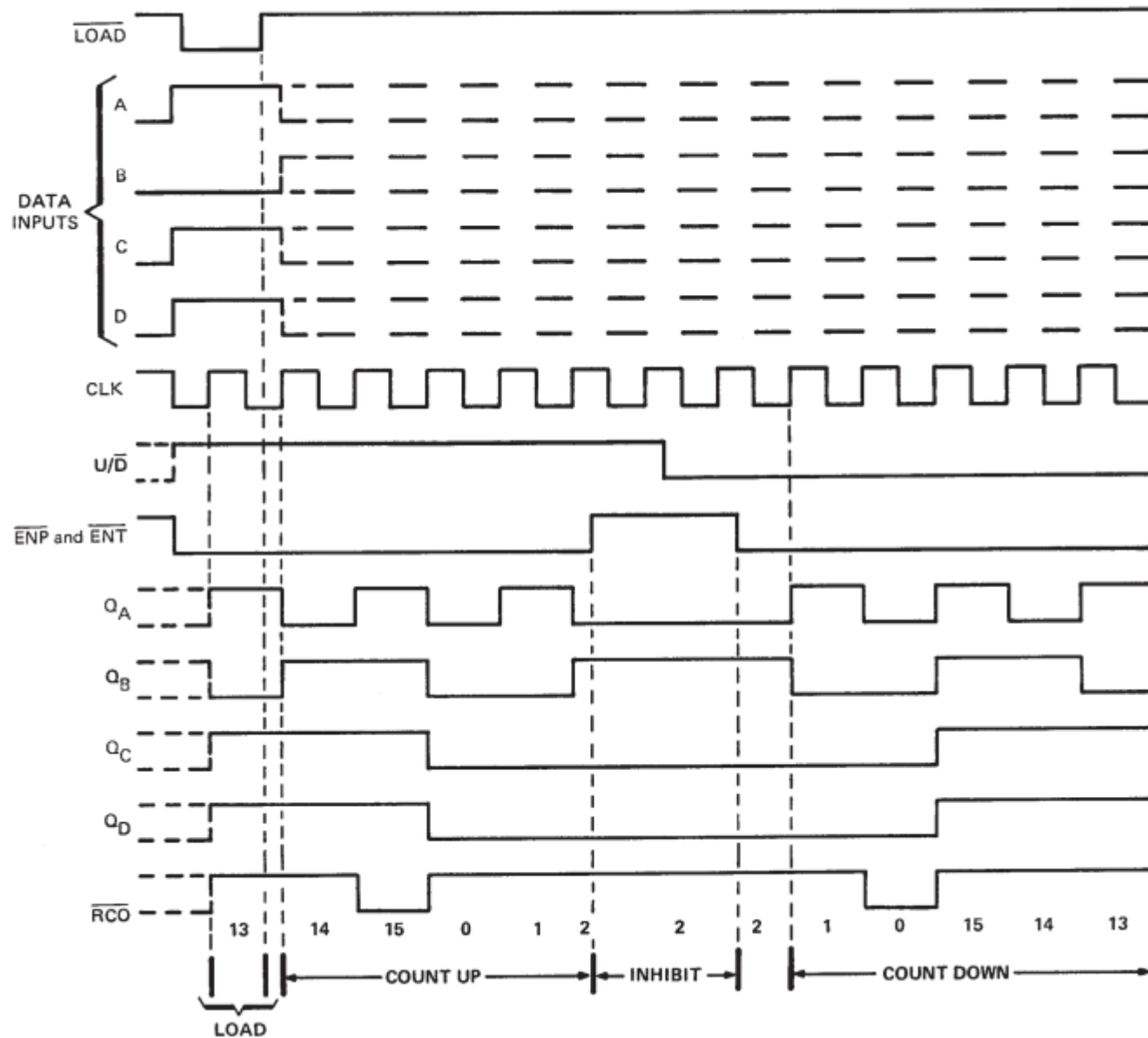


Frequency Division (Modulo N Counter)

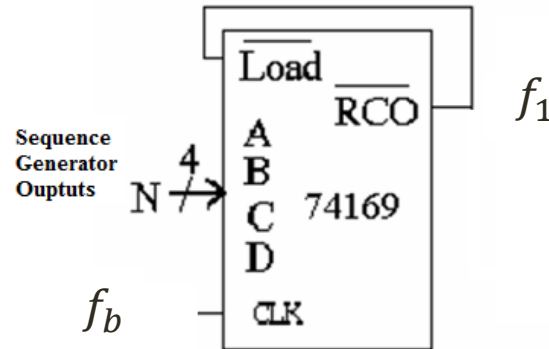


- A modulo-N counter 74169 can be used as a frequency divider,
- $f_1 = \frac{f_b}{N+1}$, $1 \leq N \leq 15$ (for Down counting)
- $f_1 = \frac{f_b}{16-N}$, $0 \leq N \leq 14$ (for Up counting)
- When U/\bar{D} is Low, the counter is counting down and up counting when it is high.

Frequency Division (T-FF)

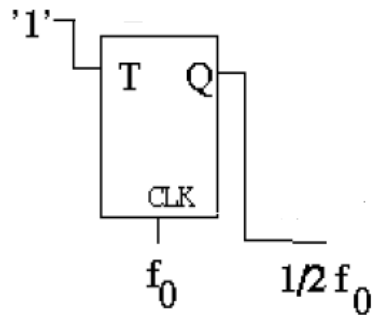

T	Q
0	Q
1	\bar{Q}

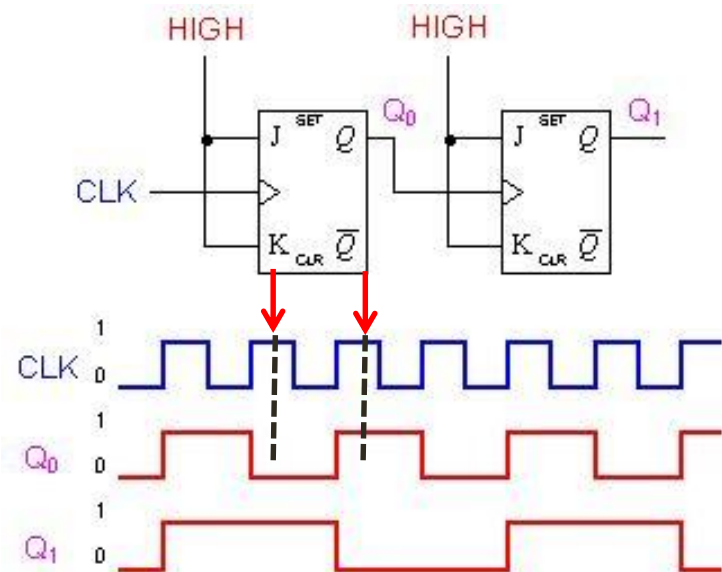

Correct the output waveform duty cycle to 50% by connecting with T-FF.

By Using a T flip flop we can divide the frequency by 2.

The T flip flop should be designed using a JK (7476) Flip Flop. (FF Conversion)

