 


# Lab 5 A

- Counter, 8 Bit Register and BCD Circuit
  - i. Counter
    - Design a 3 Bit Up Counter with Reset.
  - ii. 8 Bit Register
    - Design a 8 Bit Register which stores and outputs a 8 bit binary input on clock rising edge with 'High' on Load Input.
  - iii. Design a ckt to decode a 8 bit binary to BCD.

# Counter Design Example

- Design a 3 bit up counter which counts 0,1,2,3 and 4 once reset, it goes back to zero.



# Counter Design Example

PS	NS	
<i>CBA</i>	R=0 <i>C<sup>+</sup>B<sup>+</sup>A<sup>+</sup></i>	R=1 <i>C<sup>+</sup>B<sup>+</sup>A<sup>+</sup></i>
000	001	000
001	010	000
010	011	000
011	100	000
100	100	000

		BA			
		00	01	11	10
CR	00	1	0	0	1
	01	0	0	0	0
	11	0	x	x	x
	10	0	x	x	x

$$A^+ = \bar{A} \bar{C} \bar{R}$$


		BA			
		00	01	11	10
CR	00	0	1	0	1
	01	0	0	0	0
	11	0	x	x	x
	10	0	x	x	x

$$B^+ =$$

		BA			
		00	01	11	10
CR	00	0	0	1	0
	01	0	0	0	0
	11	0	x	x	x
	10	1	x	x	x

$$C^+ =$$


# Counter Block Diagram

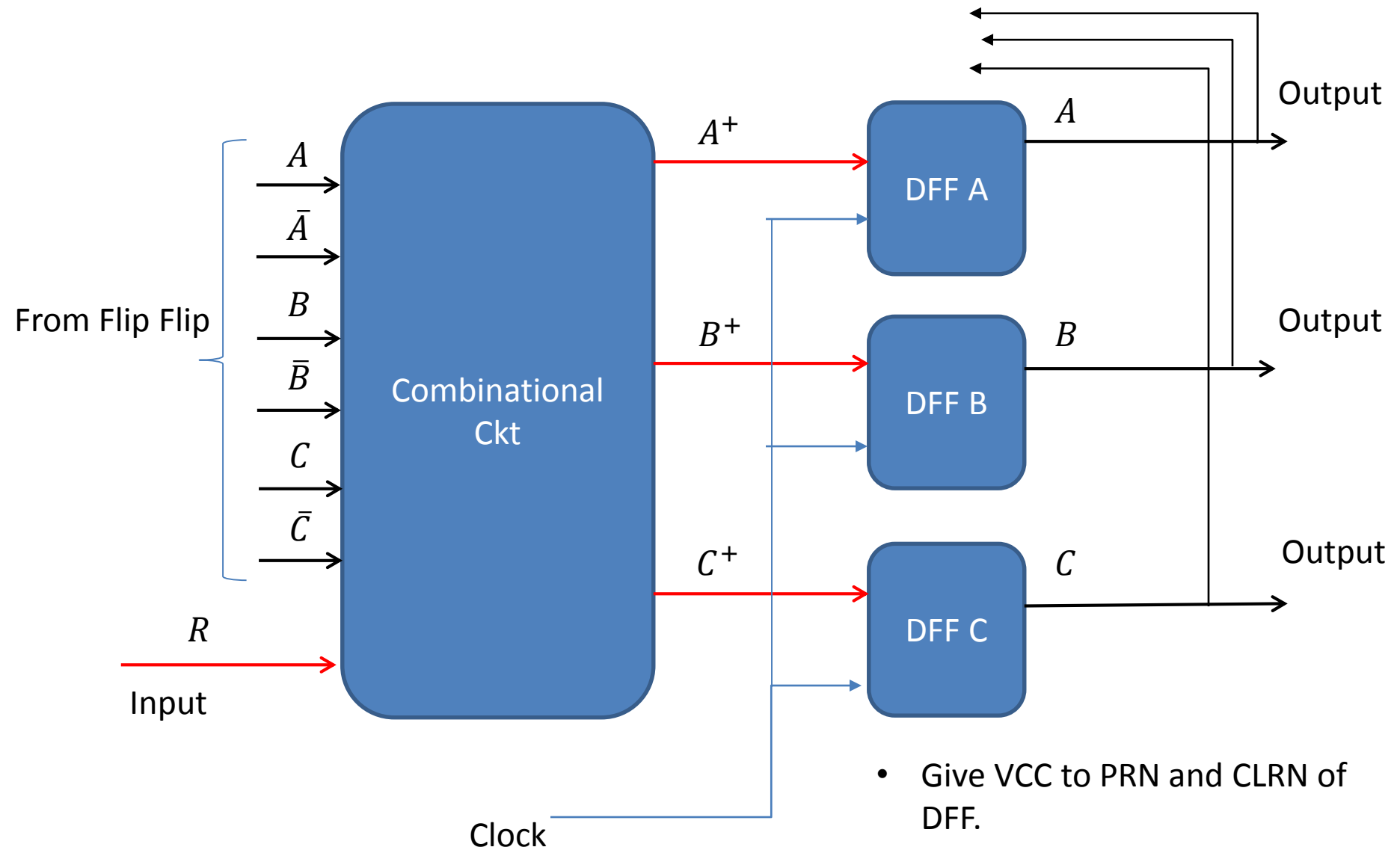
 
# A 8 bit Register Using Dff


- A register is a storage or memory component in a digital ckt.

- If (clock rising edge and Load = '1')
  - Output = input;
- Else
  - Output = Prev\_Output;
- End if;



# D Flip Flop


D	Clk	Q+
x	0	No change
1	Rising Edge	1
0	Rising Edge	0

 


# Modified D Flip Flop

- Modify D FF with an extra input: Load.

D	Clk	Load	Q+
x	0	0	No change
x	Rising Edge	0	No Change
1	Rising Edge	1	1
0	Rising Edge	1	0

 


# Register Block Diagram

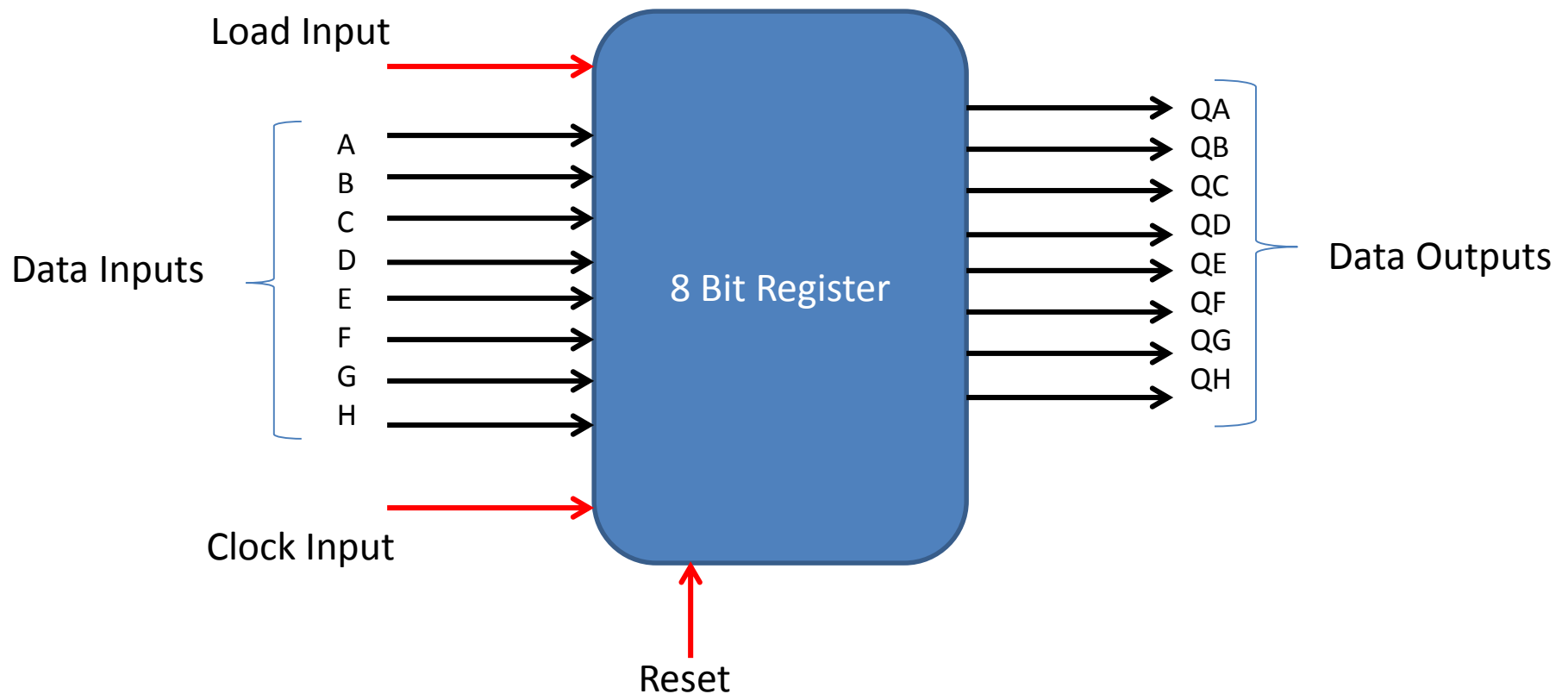




# 8 Bit Register

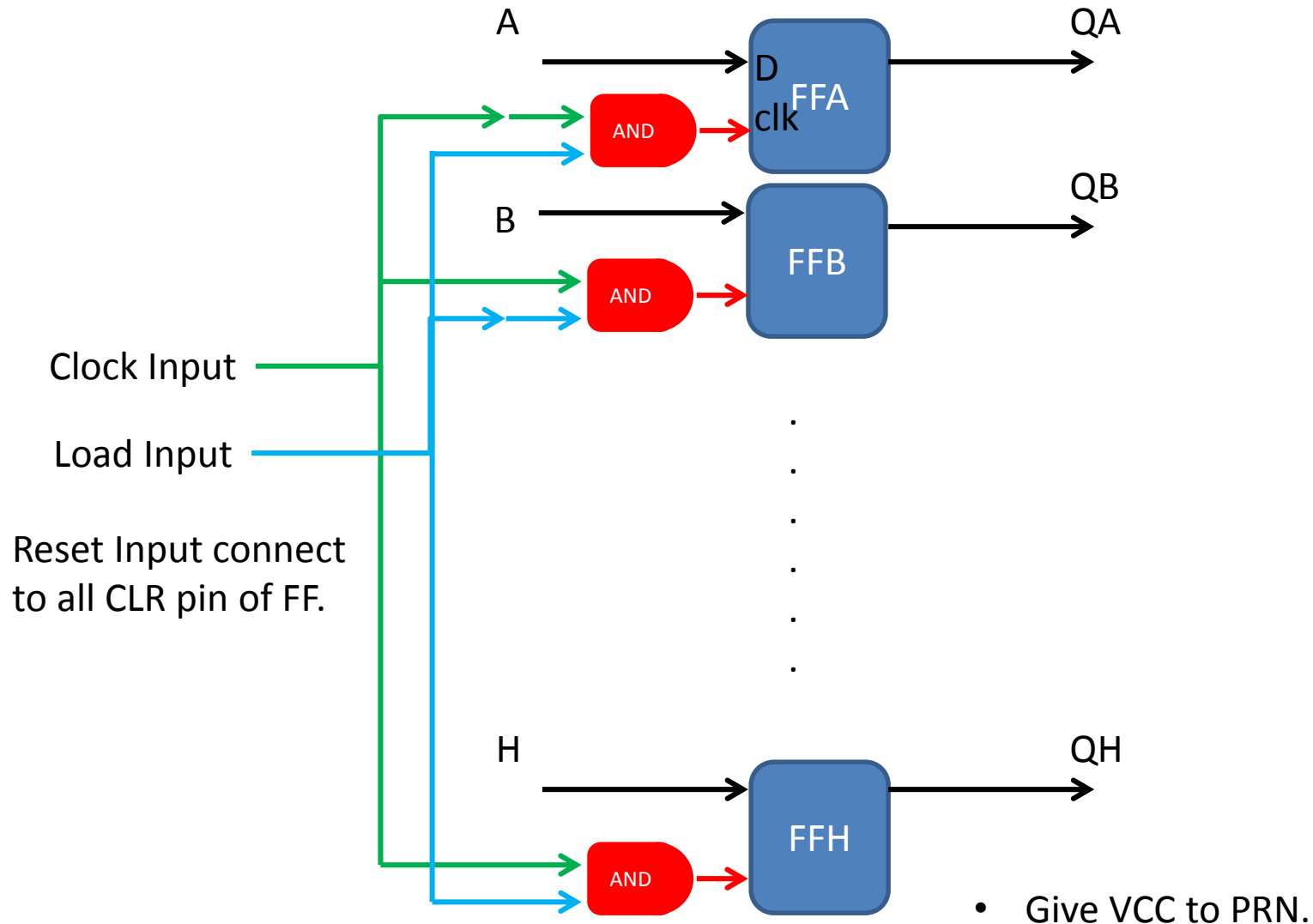
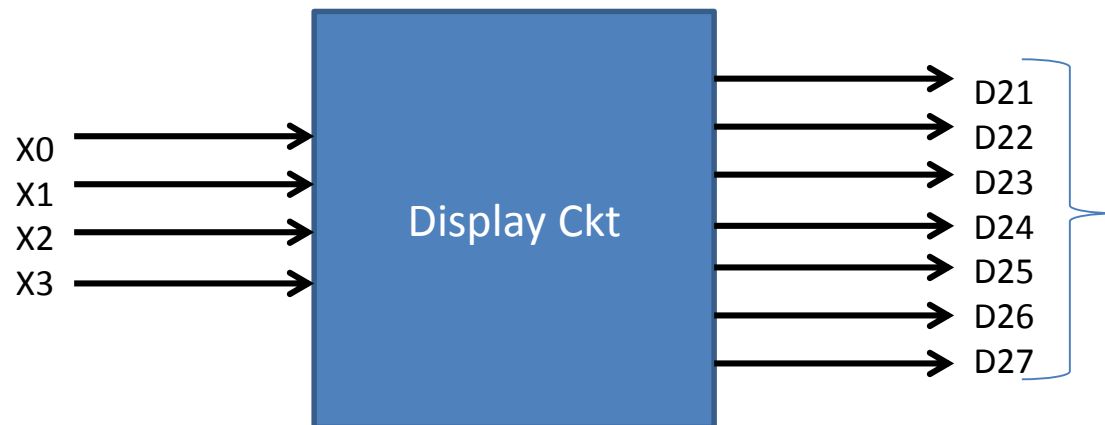
# Modify Display Ckt

- First, modify your 7 segment display ckt to 4 inputs - 7 outputs. (Just Delete the Display output (D10-D16)).



# BCD

- A BCD is a binary system which represents one decimal number with 4 binary number.
  - 15  $\rightarrow$  1111 (in Binary)
  - 15  $\rightarrow$  0001 0101 (in BCD)
- Implement a ckt that convert a 8 bit binary input to two BCD.
- Maximum binary the ckt can decode is 99.
- When the input is higher than 99, overflow = '1'.

# BCD: Binary Coded Decimal

Binary Number	BCD Outputs		OverFlow
	$U_3U_2U_1U_0$	$L_3L_2L_1L_0$	
0000 0001	0000	0001	0
.			.
.			.
.			.
0000 1001	0000	1001	0
0000 1010	0001	0000	0
0000 1011	0001	0001	0
0000 1100	0001	0010	0
.			.
.			.
.			.
0110 0011	1001	1001	0
0110 0100	xxxx	xxxx	1


# Shift Add 3 Alg

- Do 8 times ( for 8 bin binary input).
- 1. Shift left one to the binary input.
- 2. Add 3 to BCD if its greater than 5.
- 3. Go to 1.


# Example

$$(99)_{10} = (01100011)_2 = (1001\ 1001)_{BCD}$$

		BCD								Binary							
	OF	U3U2U1U0				L3L2L1L0											
		2^3	2^2	2^1	2^0	2^3	2^2	2^1	2^0	0	1	1	0	0	0	1	1
Shift 1		0	0	0	0	0	0	0	0	1	1	0	0	0	1	1	
Shift 2		0	0	0	0	0	0	0	1	1	0	0	0	1	1		
Shift 3		0	0	0	0	0	0	1	1	0	0	0	1	1			
Shift 4		0	0	0	0	0	1	1	0	0	0	1	1				
Add- 3						0	0	1	1								
		0	0	0	0	1	0	0	1	0	0	1	1				
Shift 5		0	0	0	1	0	0	1	0	0	1	1					
Shift 6		0	0	1	0	0	1	0	0	1	1						
Shift 7		0	1	0	0	1	0	0	1	1							
Add 3						0	0	1	1								
		0	1	0	0	1	1	0	0	1							
Shift 8		1	0	0	1	1	0	0	1								



9



9



# Add 3 Ckt

- If Input > 5
- Output = Input + 3;
- Else
- Output = Input;
- End

Input = 0101 (which is greater than 4)  
 Output = 0101 + 0011 = 1000

Input DCBA	Output QDQCQBQA
0000	0000
0001	0001
0010	0010
0011	0011
0100	0100
0101	1000
0110	1001
0111	
1000	
1001	
1010	xxxx
.	.
.	.
1111	xxxx

When  $input \leq 4$ .


Fill these outputs

When input > 9,  
 don't care.



 
# Add 3 Ckt

- Complete the Truth Table from prev slide
- Find the Boolean expression for QD, QC, QB and QA.
- Implement the Ckt.




		BCD								Binary							
	OF	U3U2U1U0				L3L2L1L0											
		0	0	0	0	0	0	0	0	H	G	F	E	D	C	B	A
Shift 1		0	0	0	0	0	0	0	H	G	F	E	D	C	B	A	
Shift 2		0	0	0	0	0	0	H	G	F	E	D	C	B	A		
Shift 3		0	0	0	0	0	H	G	F	E	D	C	B	A			
		If 0HGF > 5, I H1 G1 F1= 0HGF + 0011															
		0	0	0	0	I	H1	G1	F1	E	D	C	B	A			
Shift 4		0	0	0	I	H1	G1	F1	E	D	C	B	A				
		If H1 G1 F1 E > 5, H2 G2 F2 E1 = H1 G1 F1 E + 0011															
		0	0	0	I	H2	G2	F2	E1	D	C	B	A				
Shift 5		0	0	I	H2	G2	F2	E1	D	C	B	A					
		If G2 F2 E1 D > 5, G3 F3 E2 D1= G2 F2 E1 D + 0011															
		0	0	I	H2	G3	G3	E2	D1	C	B	A					
Shift 6		0	I	H2	G3	F3	E2	D1	C	B	A						
		If I H2 G3 > 5, J I1 H3 G4 =I H2 G3 + 0011															
		If F3 E2 D1 C > 5, F4 E3 D3 C1= F3 E3 D1 C+ 0011															
		J	I1	H3	G4	F4	E3	D2	C1	B	A						
Shift 7		I1	H3	G4	F4	E3	D2	C1	B	A							
		If I1 H3 G4 F4 > 5, I2 H4 G5 F5 = I1 H3 G4 F4 + 0011															
		If E3 D2 C1 B > 5, E4 D3 C2 B1 = E3 D2 C1 B + 0011															
		I2	H4	G5	F5	E4	D3	C2	B1	A							
Shift 8	I2	H4	G5	F5	E4	D3	C2	B1	A								

# BCD Alg

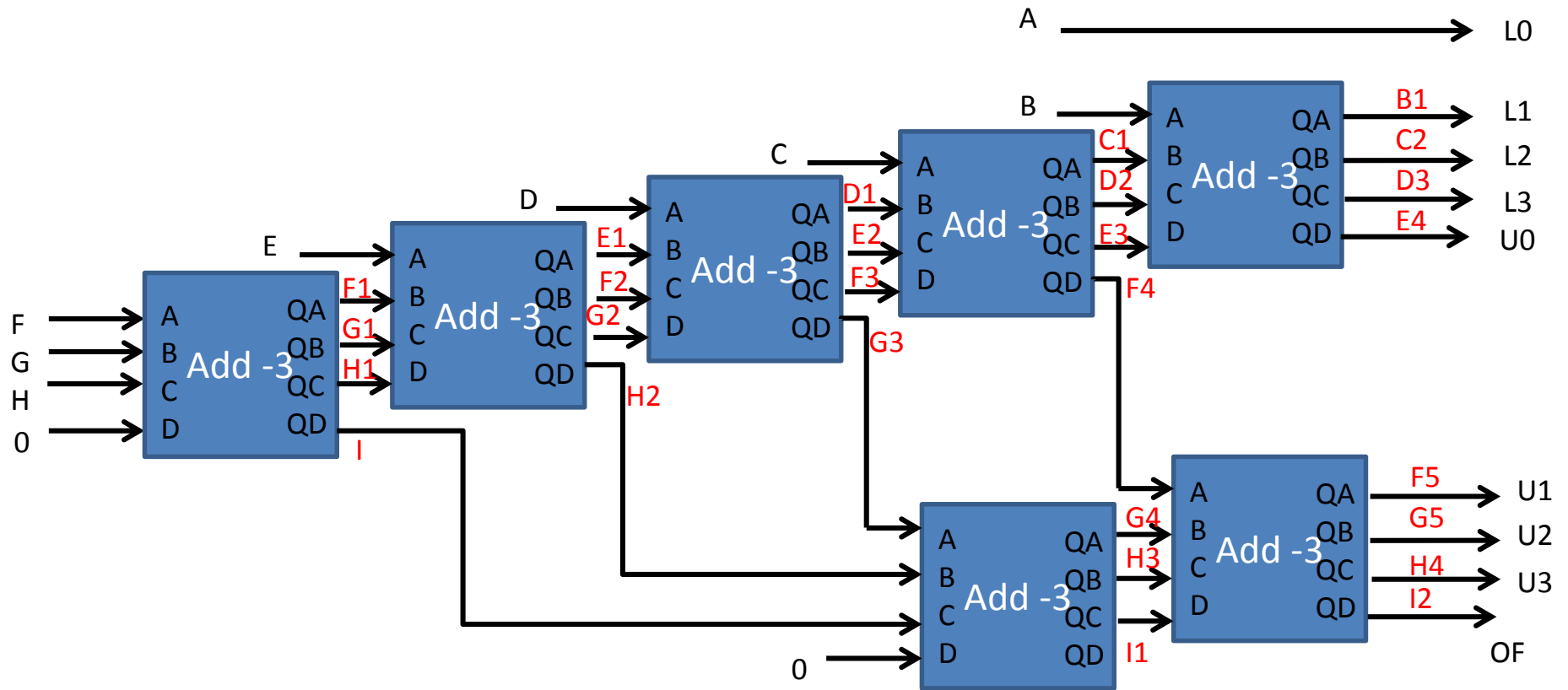


Ignore QD here!!!

# BCD Circuit Block Diagram

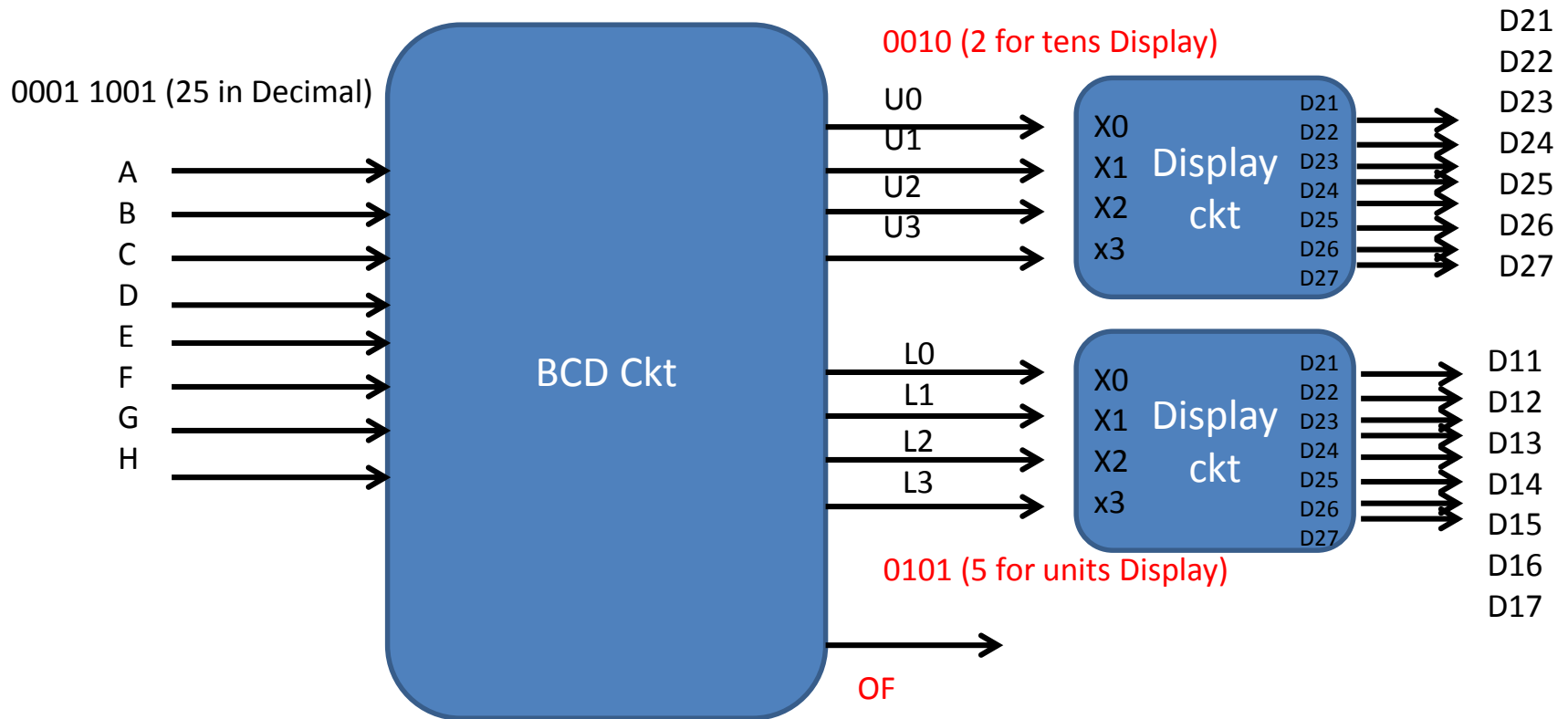

# BCD TopLevel

 

# Simulation and Downloading

- Simulation Waveform for Counter and 8 bit Shift Register.
- Download BCD Ckt to DE 2 Board.